

# Lesson 17

## Operational Amplifiers (Op Amps)

The operational amplifier (Op Amp) is one of the most versatile devices available, and applications using this device are widespread in both the analogue and digital arenas. The vacuum tube Op Amp was invented by Karl Dale Swartzel Jr (1907 – 1998) in 1941 when working at Bell Laboratories.

Looking at the Op Amp as a black box, there are usually five connections. The symbol for the Op Amp is a sideways triangle (Figure 1).

In some drawings, the power connections are not shown, but implied.

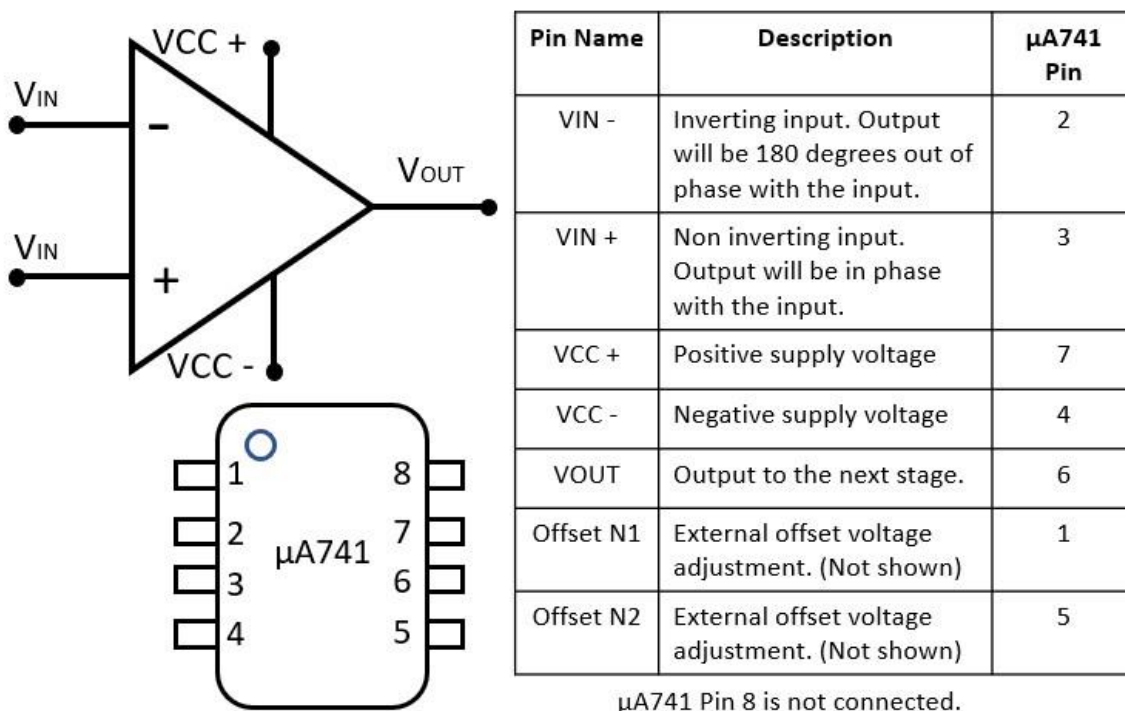


Figure 1: Op Amp connections.

### Offset

Unavoidable mismatches in the Op Amp circuitry can cause the device to output a signal when there is no input signal. These input mismatches can be adjusted as per the datasheet for the Op Amp in use. Usually by applying an offset voltage to N1 and/or N2.

### Op Amp Configurations

Open Loop – In the open loop configuration the Op Amp gain is so great it is not effective as an analogue amplifier. This configuration is ideal to use the Op Amp as a comparator or switch.

Closed Loop – The closed loop amplifier has feedback applied to the input. The feedback components control the gain of the amplifier.

### Ideal Op Amp Characteristics

*Open Loop Gain ( $A_{vo}$ )* – The ideal Op Amp has high gain of about 20,000 to 200,000. Feedback is applied to control the Op Amp gain.

*Input impedance ( $Z_{IN}$ )* – The input impedance is the ratio of input voltage to input current and is assumed to be infinite.

*Output impedance ( $Z_{OUT}$ )* - The output impedance of the ideal operational amplifier is assumed to be zero, but in reality, the output impedance is in the 100  $\Omega$ -20 k $\Omega$  range.

*Bandwidth (BW)* - An ideal operational amplifier has an infinite frequency response from DC to daylight, so it has infinite bandwidth. In real Op Amps, the bandwidth is limited by the Gain-Bandwidth product (GB), which is equal to the frequency where the amplifier's gain becomes one.

*Common Mode Rejection Ratio (CMRR)* - CMRR is the ability of the Op Amp to reject the same signal on both inputs. This is important for the cancellation of noise common to both inputs.

*Offset Voltage ( $V_{IO}$ )* – The Op Amp output is zero when the voltage difference between the inverting and the non-inverting inputs is zero. Real Op Amps have some amount of output offset voltage.

These ideal characteristics can be summarized by the very important Golden Rules:

1. In a closed loop configuration, the output drives the  $V_{IN+}$  and  $V_{IN-}$  to be equal.
2. The inputs draw no current.

### Typical Op Amp

A very common Op Amp is the  $\mu$ A741 (Figure 1). Below are a few interesting figures from the  $\mu$ A741 data sheet that make it a versatile device.

- $V_{CC+}$  Supply maximum +15 V
- $V_{CC-}$  Supply maximum -15 V
- $V_{om}$  Output voltage swing typically +/-14 V
- $I_{cc}$  No load supply current 3.3 mA
- $T_A$  Operating free-air temperature maximum 70° C
- CMRR Typically 90 dB
- $r_i$  Input resistance typically 2 M $\Omega$
- $r_o$  Output resistance typically 75  $\Omega$

### Useful Op Amp Circuits

There are many circuits using the Op Amp as the primary component. I selected 10 to provide examples.

1. The Voltage Follower, also known as a unity gain amplifier, buffer amplifier, or isolation amplifier. This circuit is used as a buffer because it draws very little current due to the high input impedance of the amplifier, which eliminates loading effects on the preceding input circuit. The Op Amp has a gain of 1 so the output is the same as the input (Figure 2). **TIP:** Review the Golden Rules.

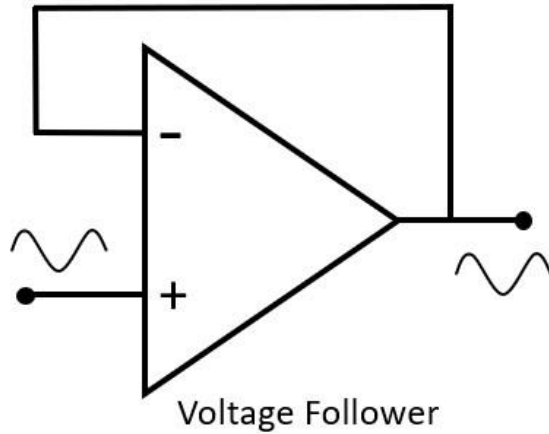


Figure 2: Voltage Follower.

2. The Inverting amplifier changes the signal by 180 degrees. The gain of the amplifier is determined by the ratio of  $R_1$  and  $R_2$  (Figure 3).

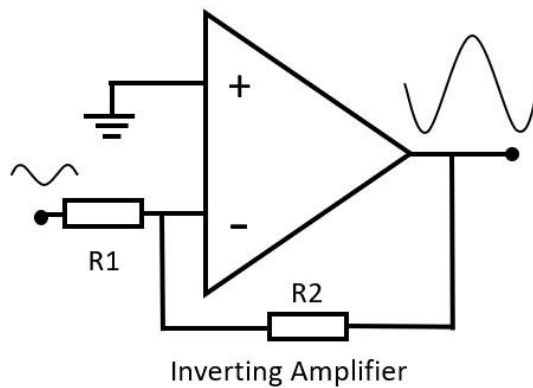


Figure 3: Inverting amplifier.

3. The Non-inverting amplifier is used where the input and output are in phase. The gain of the amplifier is determined by the ratio of  $R_1$  and  $R_2$  (Figure 4).


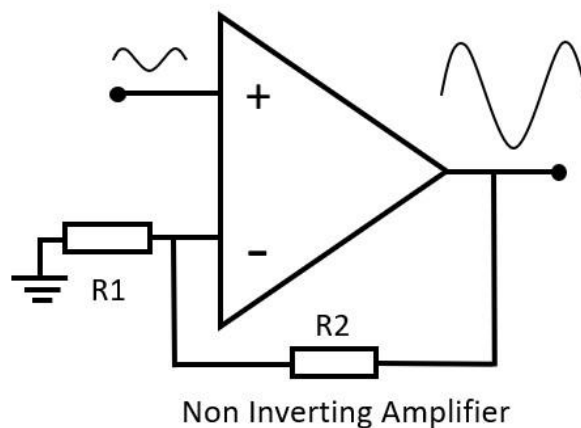


Figure 4: Inverting amplifier.

## Australian Amateur Radio Advance Licence Theory

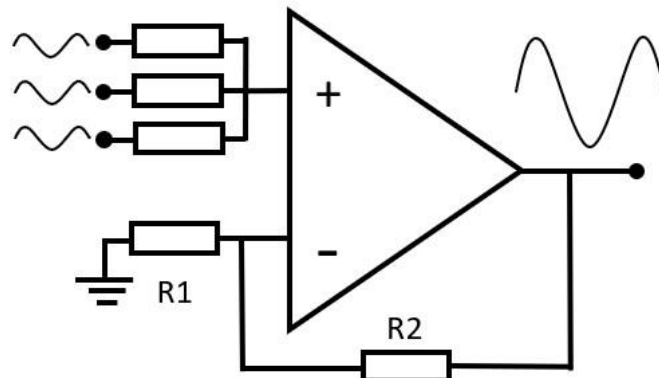4. The Non-inverting summing amplifier is used to combine the voltages present on two or more inputs into a single output voltage. As it is noninverting, the output will be in phase with the input. The gain of the amplifier is determined by the ratio of  $R_1$  and  $R_2$  (Figure 5).



Non Inverting Summing Amplifier

Figure 5: Non-inverting summing amplifier.

5. The Differential amplifier is a circuit that amplifies the difference between two input voltages but suppresses any voltage common to the two inputs. The circuit has two inputs, and the output is proportional to the difference between the two voltages (Figure 6).

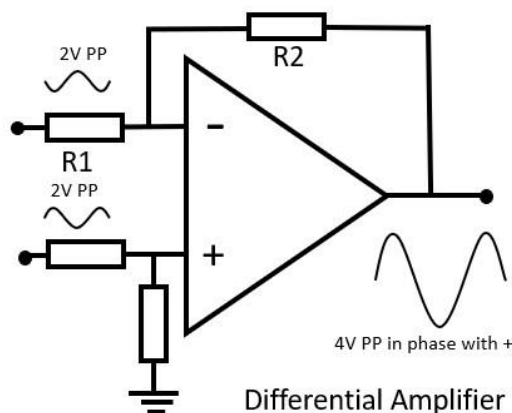


Figure 6 : Differential amplifier.

6. The Integrator Op Amp performs integration with respect to time. The output is proportional to the input voltage integrated over time governed by  $R_1$  and  $C_1$  (Figure 7).

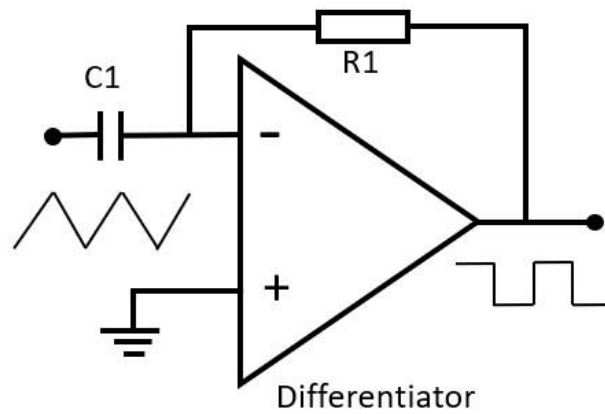


Figure 7: Integrator.

7. The Differentiator is designed so the output of the circuit is proportional to the rate of change to the input. The rate of change is governed by  $C_1$  and  $R_1$  (Figure 8).

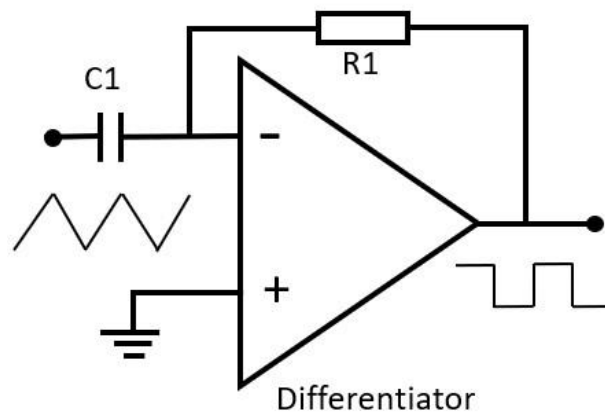


Figure 8: Differentiator.

8. THE High pass filter is a unity gain amplifier passing the frequencies higher than that determined by  $R_1$  and  $C_1$  (Figure 9).

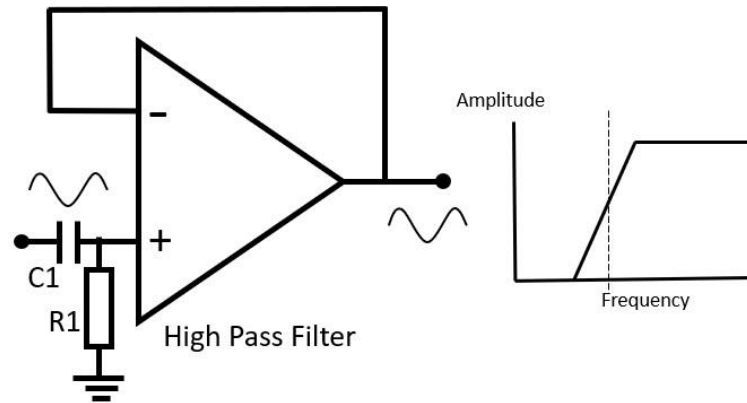


Figure 9: High Pass Filter.

9. The Low pass filter is a unity gain amplifier passing the frequencies lower than that determined by  $R_1$  and  $C_1$  (Figure 10).

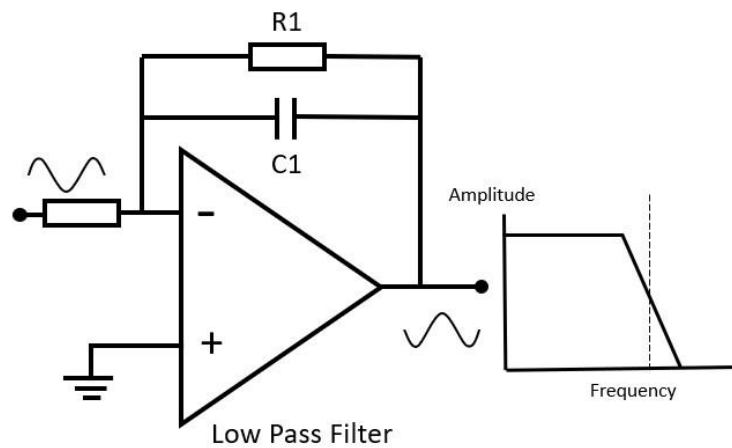


Figure 10: Low Pass Filter.

10. The Band pass filter is a unity gain amplifier.  $R_1$  and  $C_1$  determine the high pass cut off while  $R_2$  and  $C_2$  determine the low pass cut off (Figure 11).

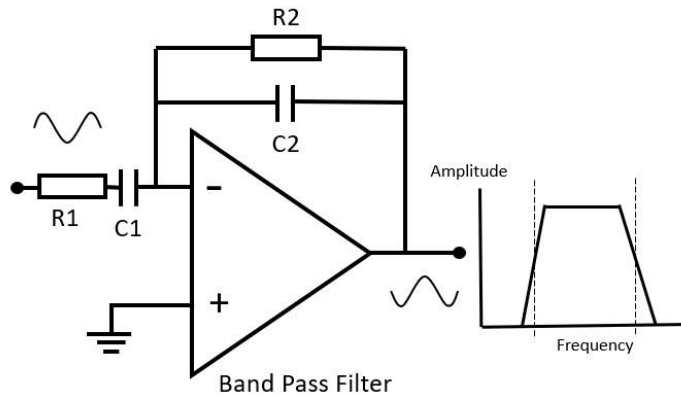


Figure 11: Band Pass Filter.

---

## INTERFERENCE AND IMMUNITY

Electromagnetic compatibility (EMC) and electromagnetic interference (EMI) are frequently referred to when discussing the regulatory testing and compliance of electronic and electrical products.

### Electromagnetic Interference (EMI)

EMI can be defined as interference that impacts the functioning of an electronic device. Sources of EMI can sometimes be environmental events but more often the EMI source is another electronic device or electrical system. Common electronic sources are transmitters, cellphones, welders, motors and LED screens.

EMI is also called RFI (Radio Frequency Interference) however EMI is any frequency of electrical noise, whereas RFI is a subset of noise on the EMI spectrum.

There are two types of RFI.

- Conducted EMI is unwanted high frequencies that ride on the AC wave form.
- Radiated EMI is emitted through the air.

### Causes of EMI

Interference occurs when an unwanted signal disrupts the use of your television, radio or cordless telephone. Interference may prevent reception altogether or may cause only a temporary loss of a signal. The interference may affect the quality of the sound or picture produced by your equipment.

The origin for any EMI may come from many sources.

- External noise – other electrical equipment nearby.
- Natural origins - electrostatic interference and electrical storms.
- Radio Frequency Interference (RFI) –radio systems signals
- Crosstalk - in cabling

### Intermodulation

Intermodulation distortion is the undesired combination of several signals in a nonlinear device which produces a new unwanted frequency. This new frequency can cause interference in

## Australian Amateur Radio Advance Licence Theory

adjacent receivers. Intermodulation can also be produced in rusty or corroded tower joints, guy wires, turnbuckles and anchor rods or any nearby metallic object acting as a nonlinear “mixer/rectifier” device.

### Eliminating EMI Influence

Methods to reduce or eliminate EMI:

**Filtering** - EMI filters can suppress electromagnetic noise transmitted through conduction. These filters extract any unwanted signals while allowing desirable signals to pass. A choke is an example of a Low Pass Filter removing EMI.

**Grounding** - Grounding devices provides a low impedance path for EMI to dissipate and can mitigate the ill-effects of EMI.

**Decoupling** – Decoupling capacitors in circuits is a good practice. Decoupling capacitors in power supplies reduce the possibility of EMI entering the device from the power mains.

**Shielding or Blocking** - EMI shielding is the practice of blocking the electromagnetic field from impacting the device. These barriers are made of conductive or magnetic materials. You will find EMI shielding in your cell phones, in the microwave oven door, as well as your computers and keyboards.

A Faraday shield is a good example of blocking EMI.

### EMC

It is rare for electronics devices to operate in isolation as they are usually engineered to function in the presence of some form of EMI. This is particularly important in military-grade, medical and avionics equipment.

EMC is a measure of a device's ability to operate as intended in its shared operating environment while not affecting the ability of other equipment within the same environment to operate as intended. They all must play together.

Testing how a device will react when exposed to electromagnetic energy is known as immunity (or susceptibility) testing. Measuring the amount of EMI generated by the device's internal electrical systems is known as emissions testing.

### Reducing Interference

- Monitor and moderate power output.
- Site your antenna from other antennas eg TV
- Avoid any frequencies that are known to cause interference in your area.
- Fit a balun to the antenna.
- Conducted interference can be removed by placing chokes on affected cables.
- Install a mains filter to prevent interference getting into the mains lines.
- Show goodwill to neighbours if problems occur.



*Have fun and stay safe.*