Jules' Workshop

Standard

Unit 20 – QUESTIONS

Q1 Why does an Op amp have a + Vin and a -Vin?

Q2 What are the two golden rules when using Op amps?

Q3 What is an open and closed loop amplifier?

Q4 What is Common Mode rejection?

Q5 What is EMI?

Q6 What is EMC?

Q7 What is an example of a natural EMI in a receiver?

Q8 What are the four basic methods for eliminating the elects of EMI on a system?

 © Jules Workshop 2026