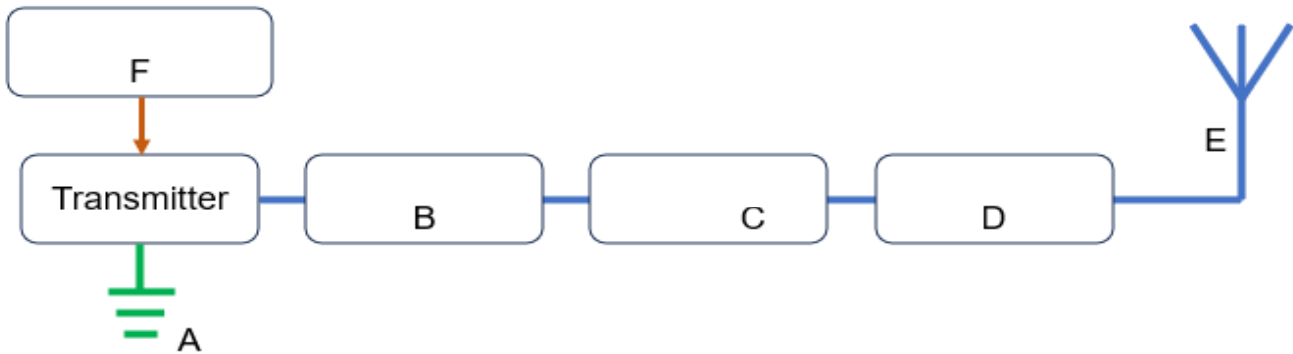


PRACTICAL

Section 7– QUESTIONS

1. Complete the names of the equipment in the diagram below.



2. In what order should this equipment be connected together?
3. In what order should this equipment be disconnected?
4. Why should this sequence be followed?